

**LTM 8045 - Inverting or SEPIC  $\mu$ Module (Power Module)**  
**DC/DC Converter with Up to 700mA Output Current**  
[\(Datasheet\)](#)


---

**IC Features:**

- Wide Input Voltage Range: 2.8V to 18V
- Up to 700 mA Output Current at  $V_{in} = 12V, V_{out} = 2.5V$  or  $-2.5V$
- Up to 375 mA Output Current at  $V_{in} = 12V, V_{out} = 15V$  or  $-15V$
- Storage Temperature :  $-55^{\circ}C$  to  $125^{\circ}C$

**Schematic:**

**Note:** The following schematic is a -5V DC/DC converter design.

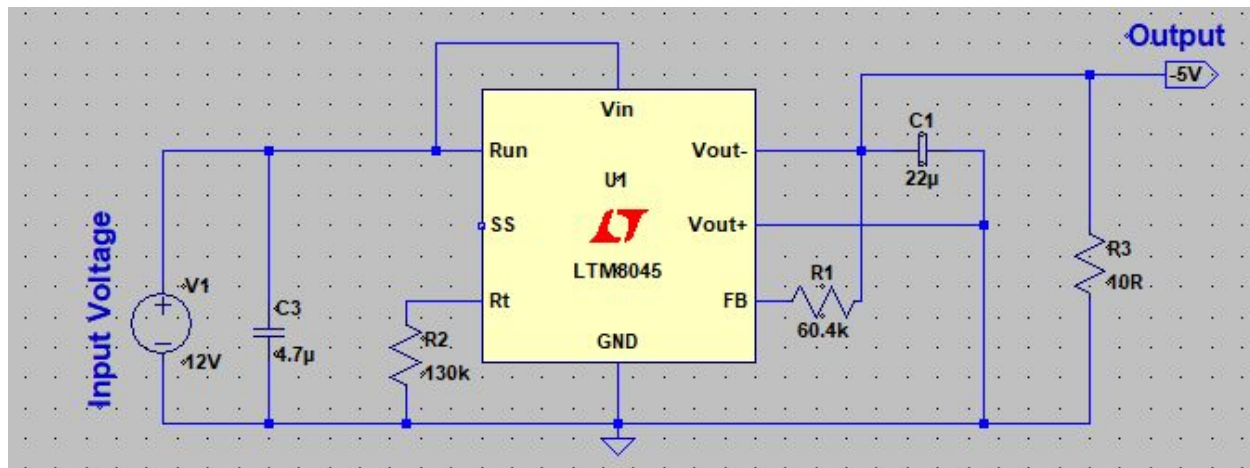

**Figure 1 : LTM8045 - DC/DC Converter design from its datasheet**

**Bill of Materials:**

- Capacitors :  $4.7\mu F/16V, 22\mu F/16V$
- $R_1: 60.4k\Omega, R_2: 130k\Omega, R_{Load}: 10\Omega, 5\Omega, 3\Omega$
- DC/DC Converter : LTM8045

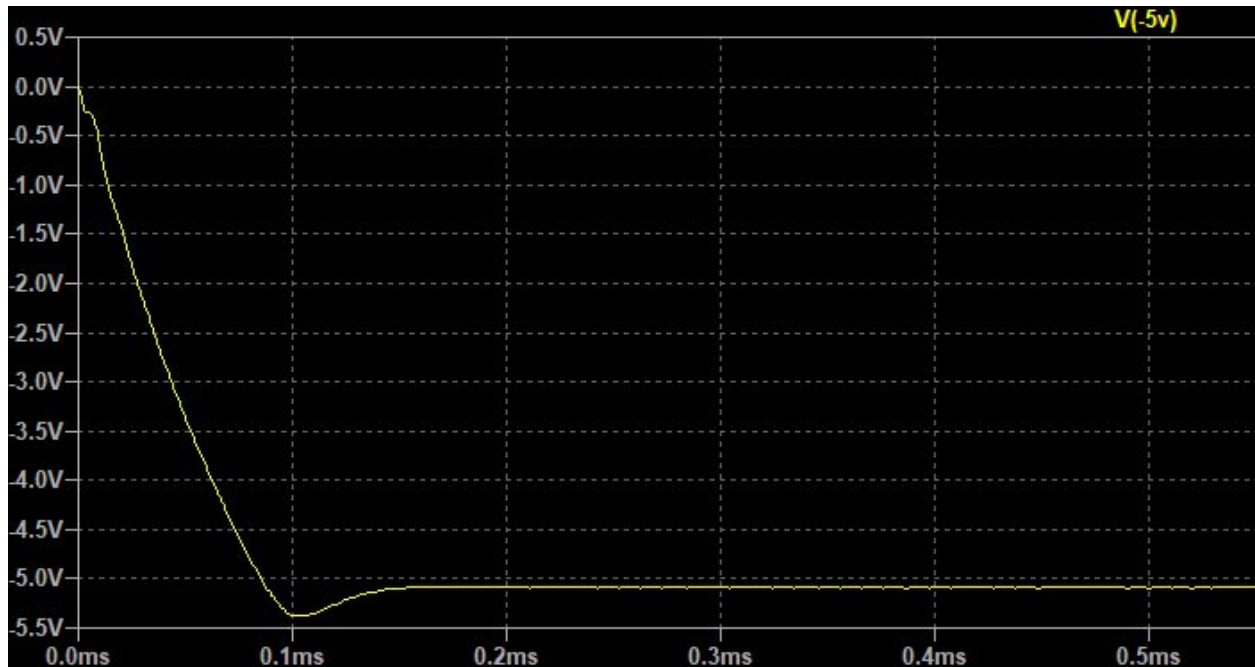


Figure 2 : LTM8045 - Converter Output Voltage when  $R_{Load} = 10 \Omega$

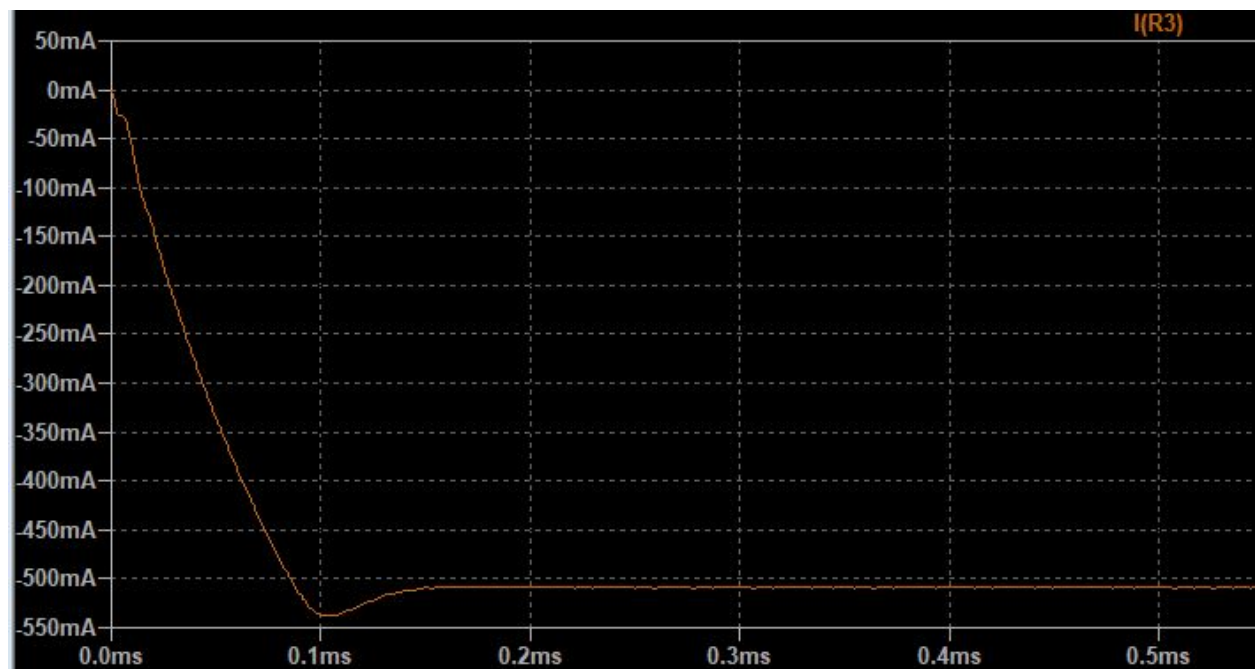


Figure 3: LTM8045 - Converter output current through  $R_{Load}$  when  $R_{Load} = 10 \Omega$

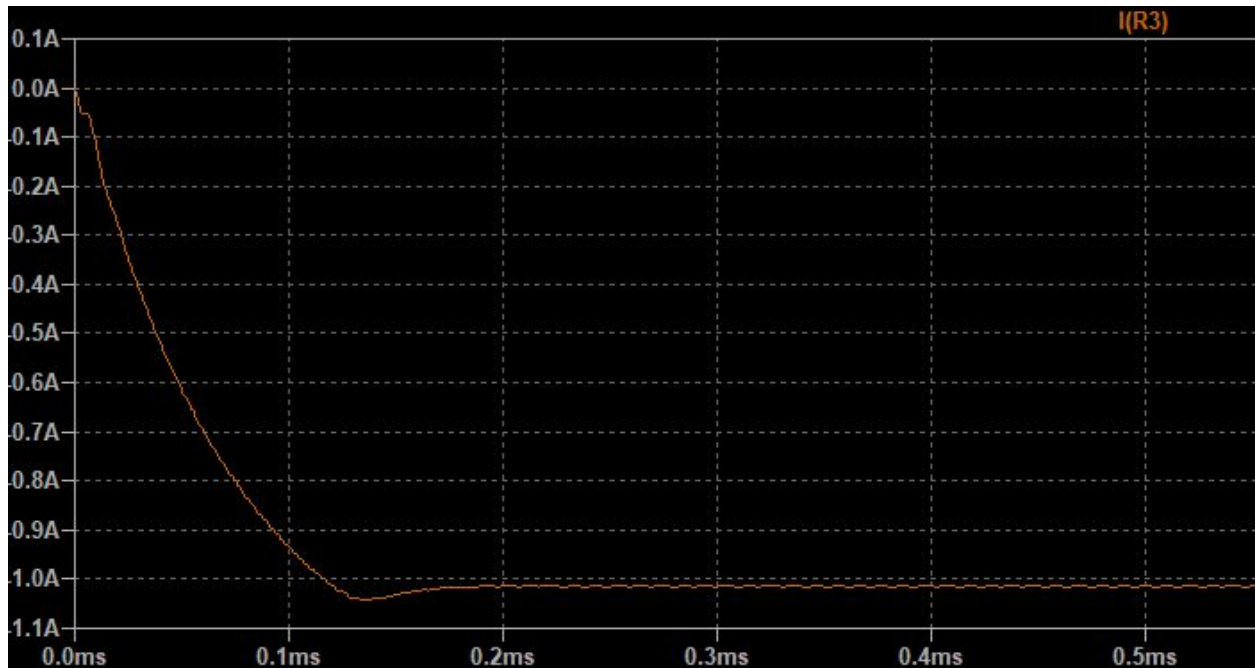


Figure 4 : LTM8045 - Converter Output Voltage when  $R_{Load} = 5\ \Omega$

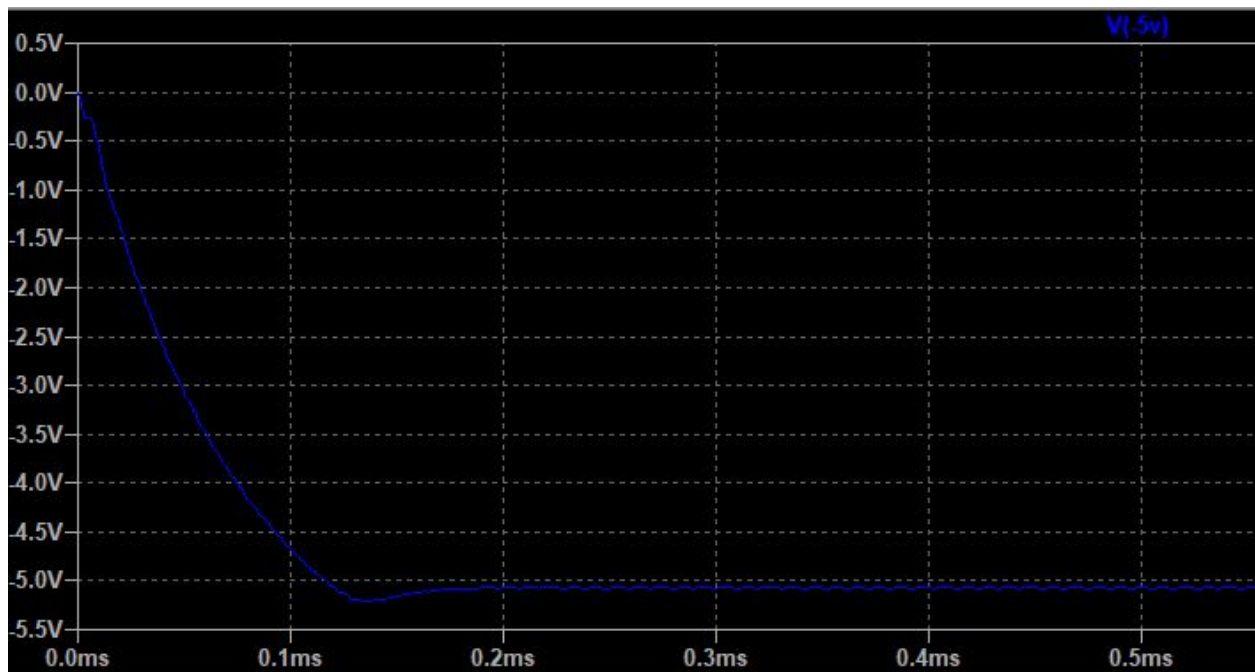


Figure 5 : LTM8045 - Converter Output Voltage when  $R_{Load} = 5\ \Omega$

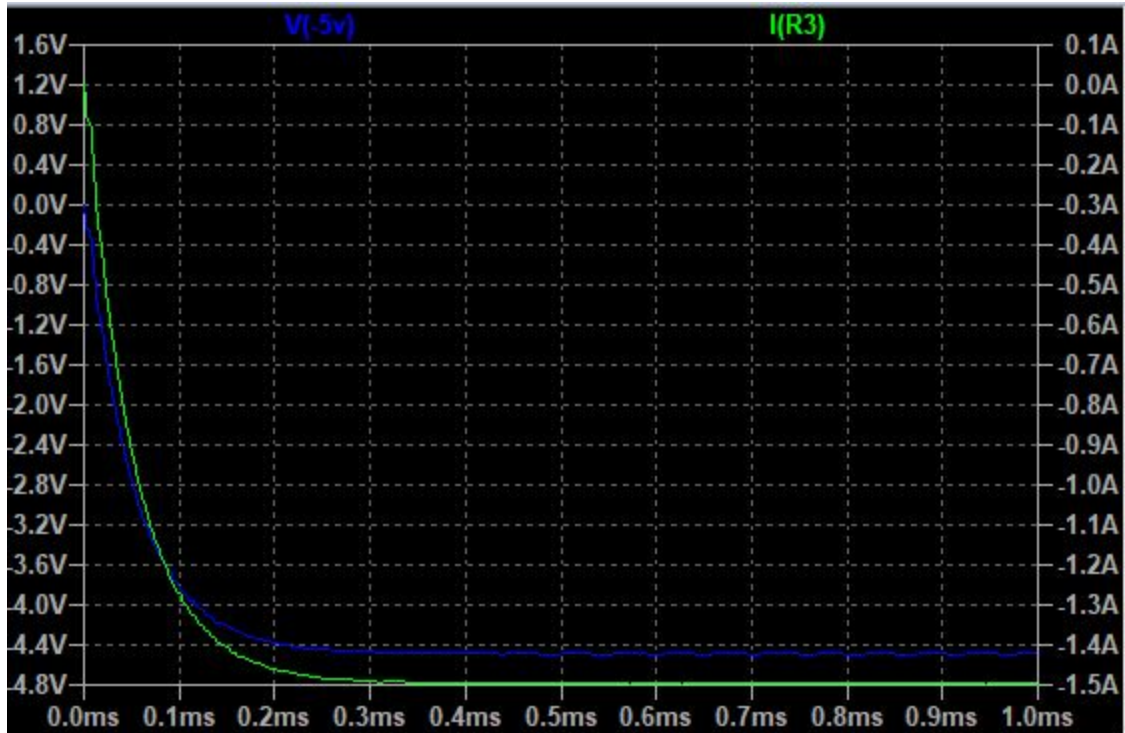


Figure 6 : LTM8045 - converter output voltage and current when  $R_{Load} = 3\Omega$

### Results:

LTM8045 was randomly picked to design a  $\mu$ Module DC/DC converter. First step in the design was of course to make the schematic of the DC/DC converter. Exactly the same components were picked in the given -5V DC/DC converter schematic, as shown in Figure 1, in the datasheet of the IC. In order to draw about 0.5A from the converter a  $10\Omega$  was placed as a load. In Figure 3, it can be seen that the peak output current at 0.1 ms was actually more than -0.5A, nearly -0.55A. This is significant and should be taken into consideration when used with actual loads other than just resistors. After 0.1 ms, the output current of the converter went to nearly -0.5A and became stable. In Figure 1, the output voltage is shown. Figure 1 and Figure 2 are actually very similar. Current and Voltage response of the converter look very alike. The converter's output voltage climbed to nearly -5.25V after 0.1 ms its powered. This is pretty much the same response as in Figure 2 since there is a relationship between voltage and current. After 0.1 ms, the output voltage went to nearly -5V as expected. In order to test the converter, the load resistor was changed to  $5\Omega$  to draw more current from it. The current and voltage response of the converter is similar but this time the peak shown in Figure 1 and Figure 2 is shifted about 0.05 ms to the right as shown in Figure 4 and Figure 5. From the converter, the nominal current drawn was 1A but at about 0.15 ms it was 1.05A. Similarly the voltage output was about -5.25V. In order to test the converter's limits, it was pushed to draw -1.66A (nominally). Expectedly, the output voltage dropped to -4.4V instead of -5V. This is unwanted. So one should be aware of how much can be drawn from the DC/DC converter.

Let's look at the performance of the converter from another point. The peak efficiency of the IC can be obtained when the output current is beyond 0.4A (with  $V_{in}$  : 12V) as shown in the efficiency plot below. When the output current is let's say 10 mA, the expected efficiency is about 7%. This is very low for efficiency. Wasted power can cause significant problems especially in battery-powered systems. Also the minimum required voltage

#### Appendix A :

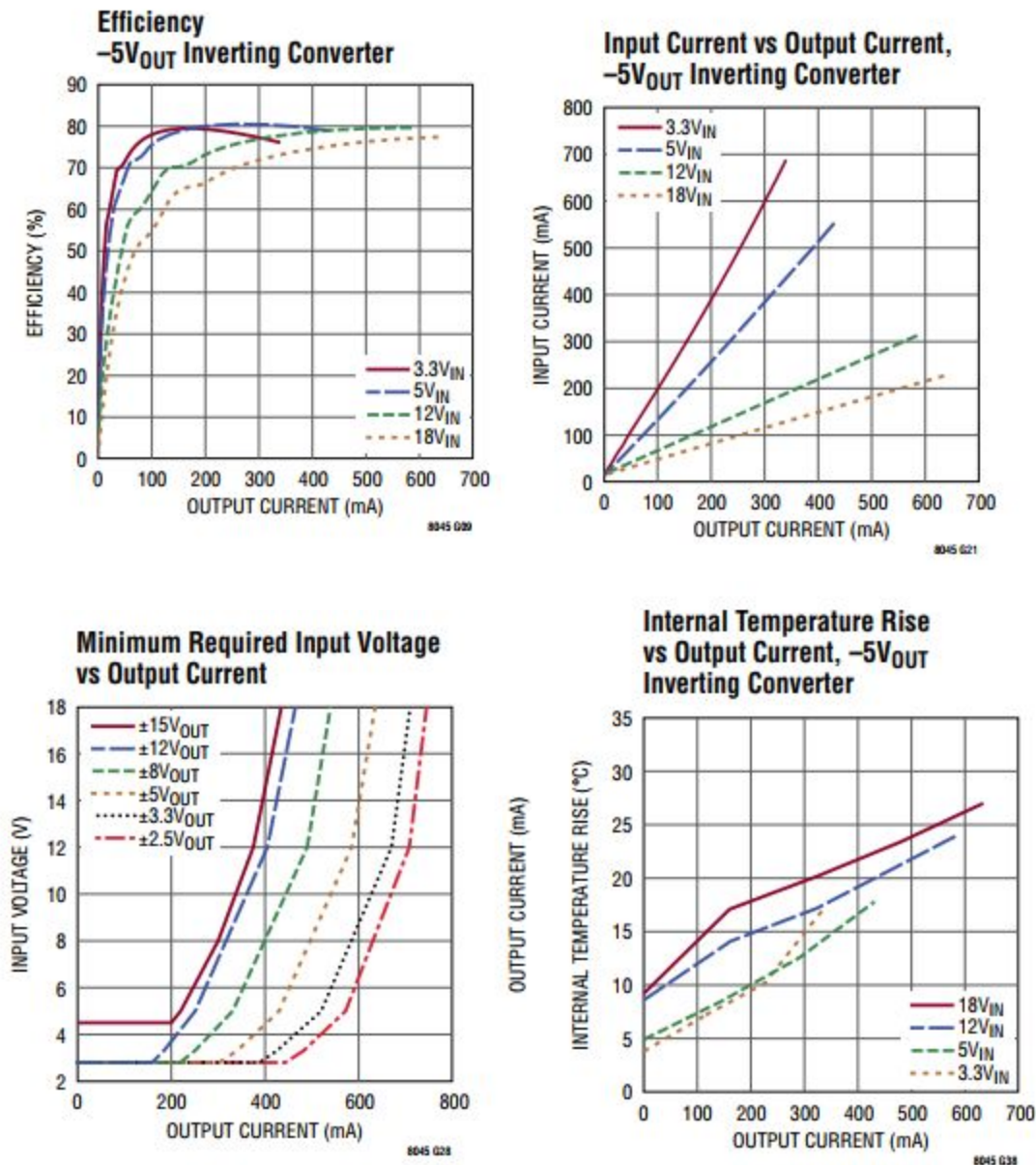


Figure A.1: LTM 8045 Performance Characteristics